
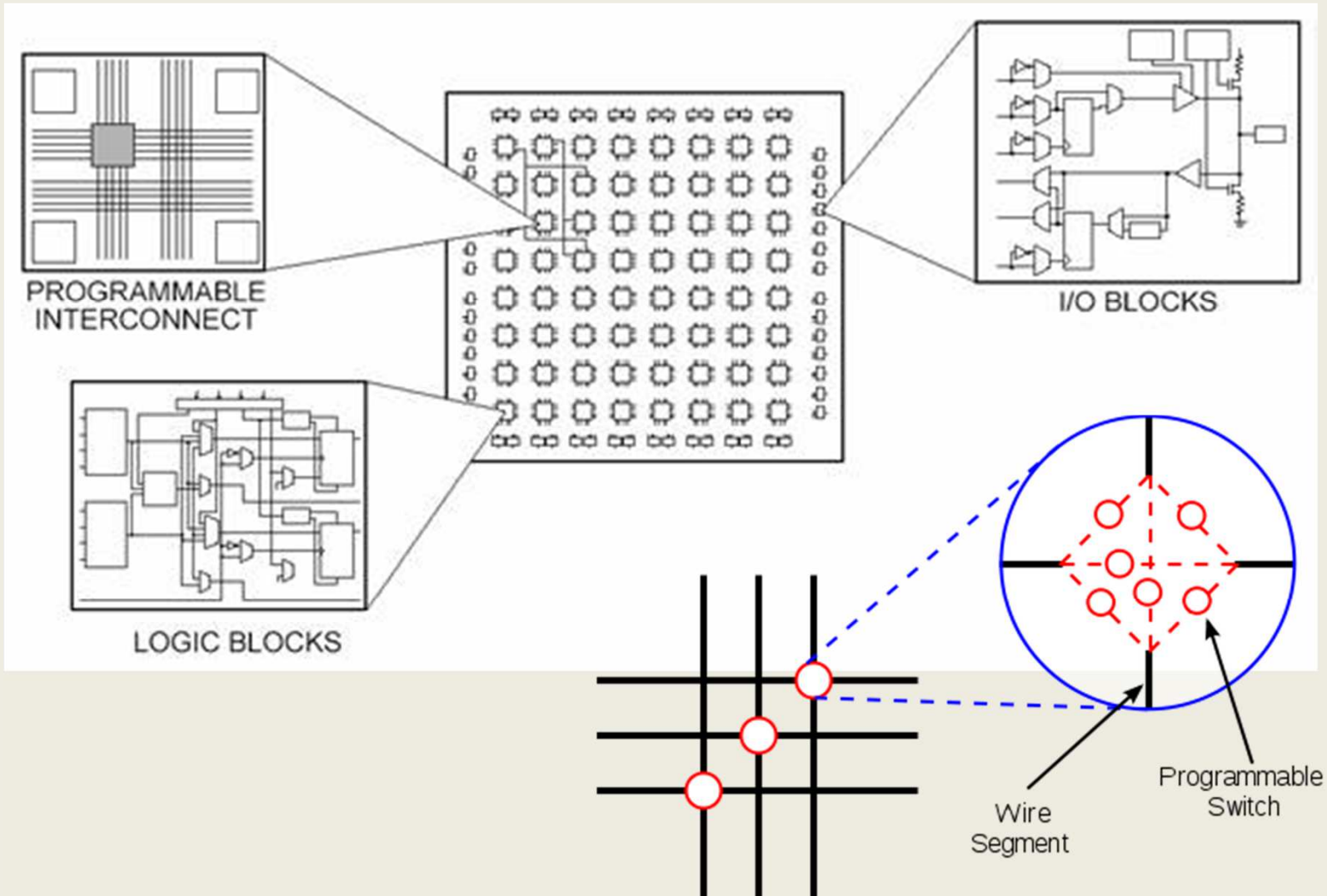


FPGA Structure

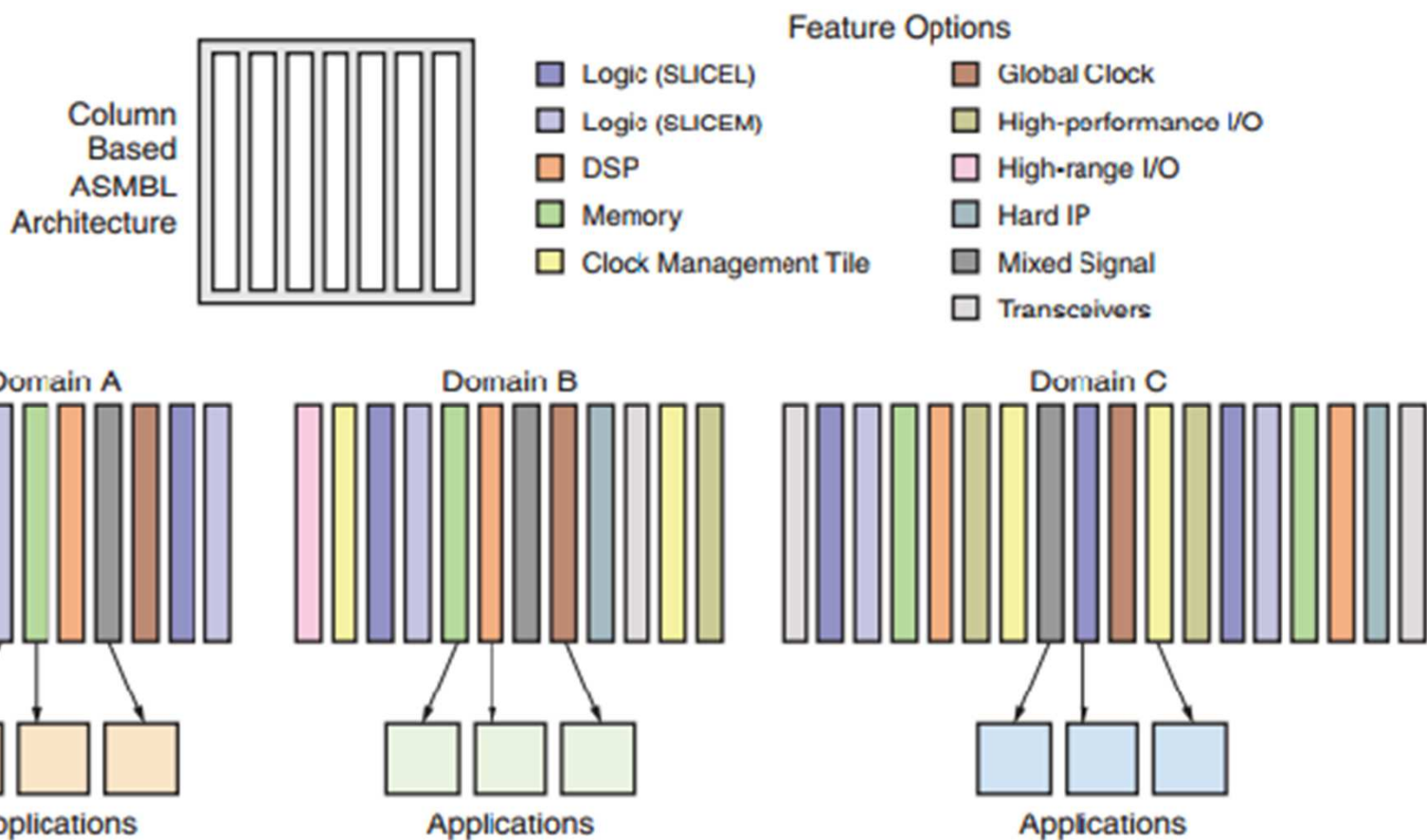



Xilinx ASMBL Architecture



Design Flow


- Synthesis: HDL to FPGA primitives
- Translate: FPGA Primitives to FPGA Slice components
- Map: Packing of Slice components into Slices, placement of Slices on fabric
- Route: connecting Slices
- Bitstream generation: generating the required configuration bits to load into the FPGA

Configurable Logic Blocks

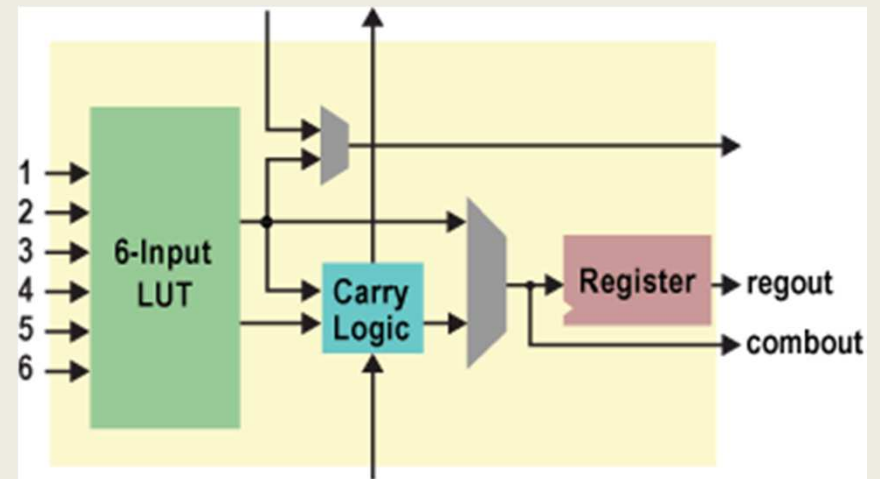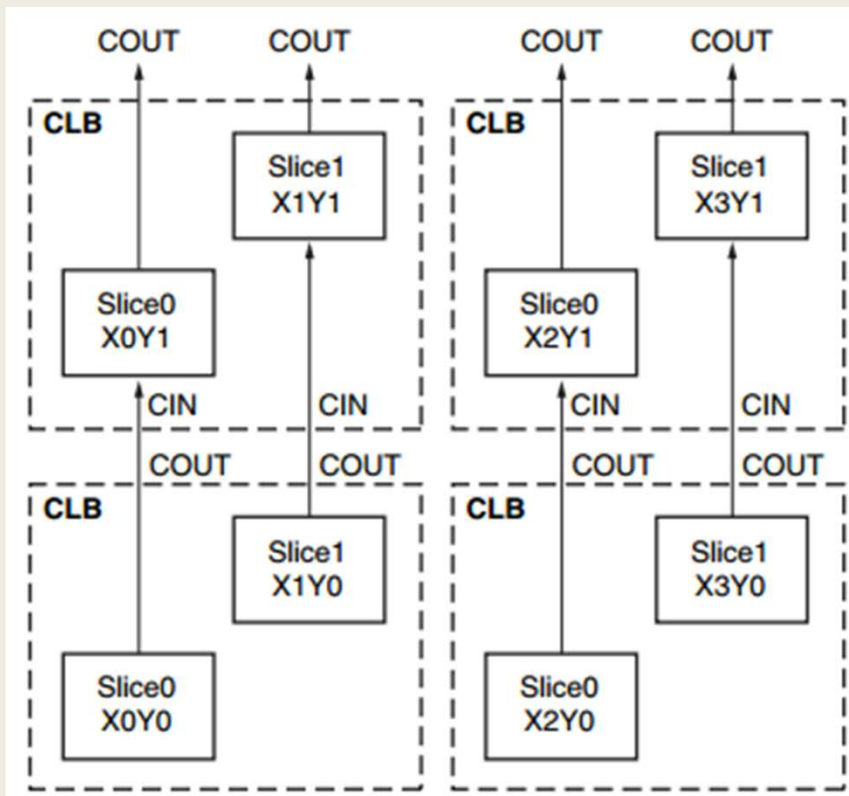


Slice LUTs

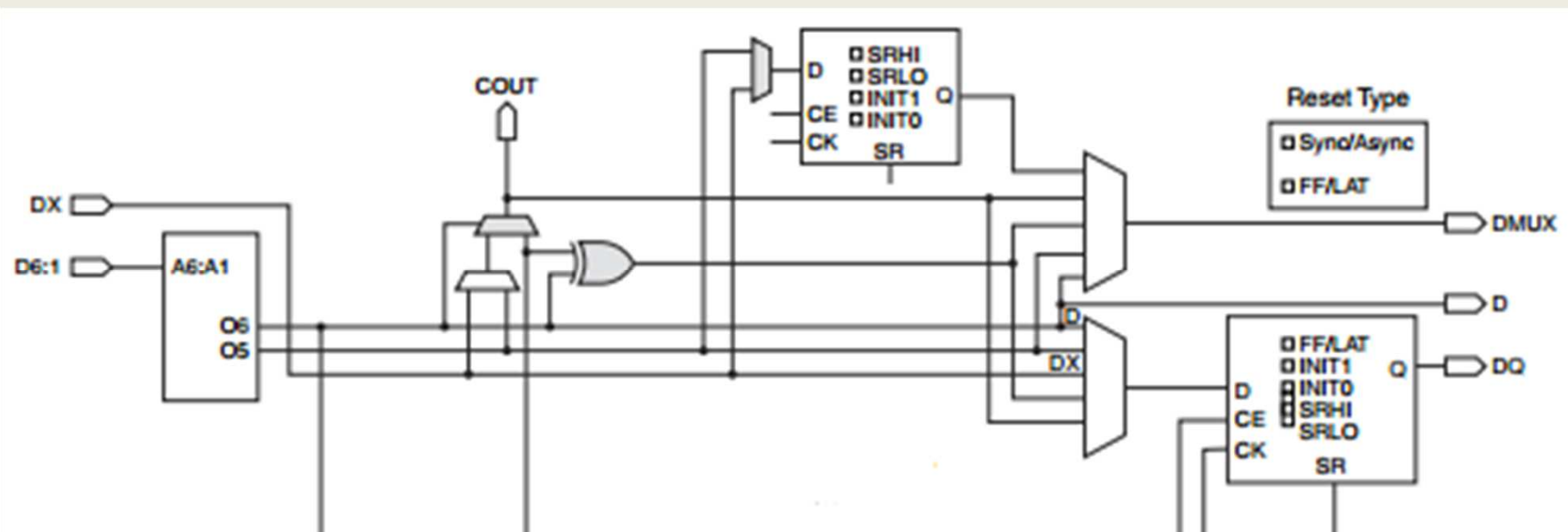- 1 CLB = 2 Slices
- 1 Slice = 4 “LUT Modules”, 2 MUXF7, 1 MUXF8
- A LUT Module contains: 1 LUT6, 1 MUXCY, 1 XORCY, 2 FFs



Slice LUTs

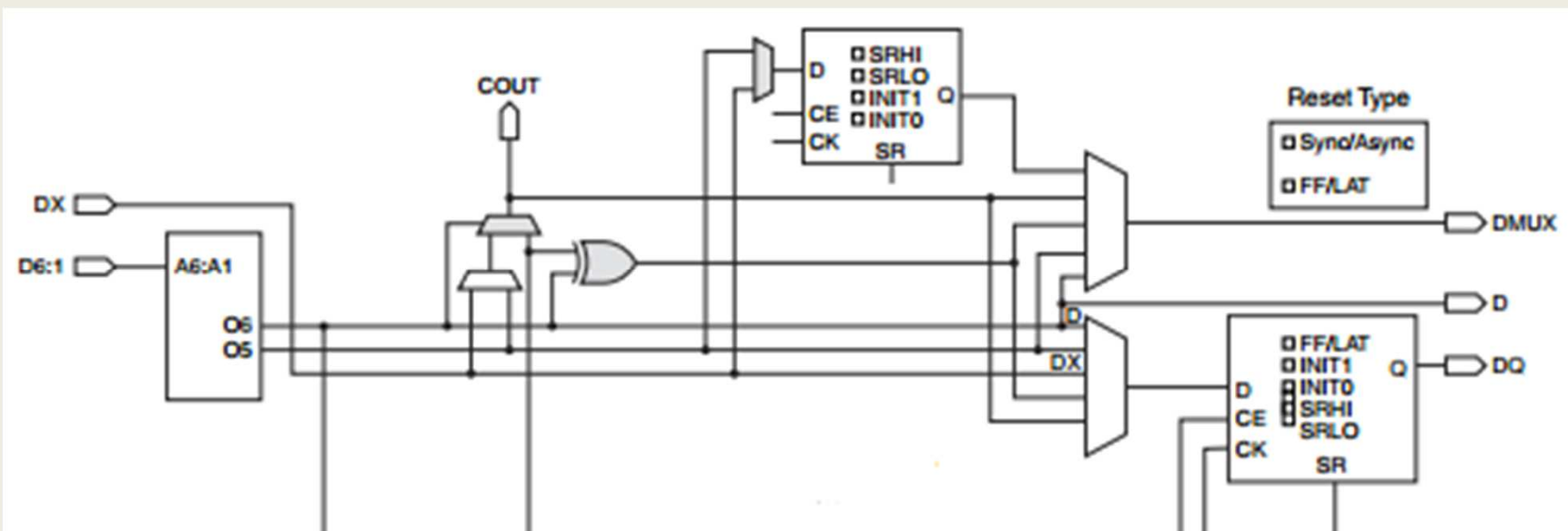
- 1 CLB = 2 Slices
- 1 Slice = 4 “LUT Modules”, 2 MUXF7, 1 MUXF8
- A LUT Module contains: 1 LUT6, 1 MUXCY, 1 XORCY, 2 FFs



Slice LUTs

- LUTs = Multiplexers
 - Data Inputs from the FPGA configuration bits
 - Selection inputs from user logic
 - For N-input LUT, 2^N configuration bits

A	B	A B
0	0	0
0	1	0
1	0	0
1	1	1

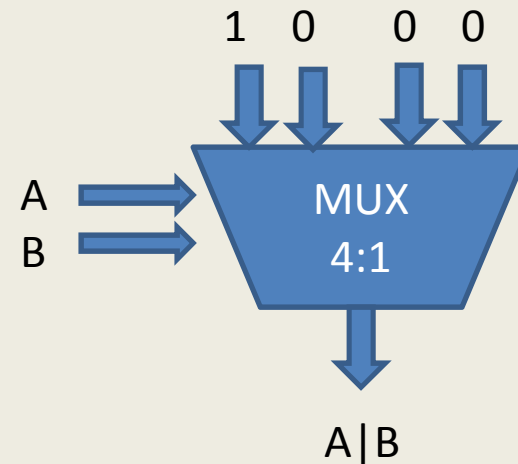

Slice LUTs

- Number of LUT inputs is architecture dependent:
 - Xilinx Virtex 4 and earlier: 4-input LUTs (LUT4), 2 LUTs per Slice
 - Xilinx Virtex 5 and later: 6-input LUTs (LUT6), 4 LUTs per Slice
 - Xilinx Virtex 6 and 7-Series: 6-input LUTs, configurable as two shared-input 5-input LUTs
 - Altera: 8-input LUTs (ALM), configurable as combinations of smaller LUTs

Area and Delay vs. LUT Size


- LUTs have constant delay, regardless of implemented function
- Example:
 - LUT4 architecture (Virtex4)
 - $O = I1 \& I2 \& I3 \& I4 \Rightarrow 1 \text{ LUT}, 0.43 \text{ ns}$
 - $O = I1 \& I2 \& I3 \& I4 \& I5 \& I6 \Rightarrow 2 \text{ LUTs}, 0.93 \text{ ns}$
- As a general rule: LUT delays are small, routing delays can be large

Exercise: Multiplexers

- Implementation of 2:1, 4:1, 8:1 multiplexers on Virtex-4 architecture
- [Advanced multiplexing techniques: XAPP522](#)

Slice Multiplexer Resources

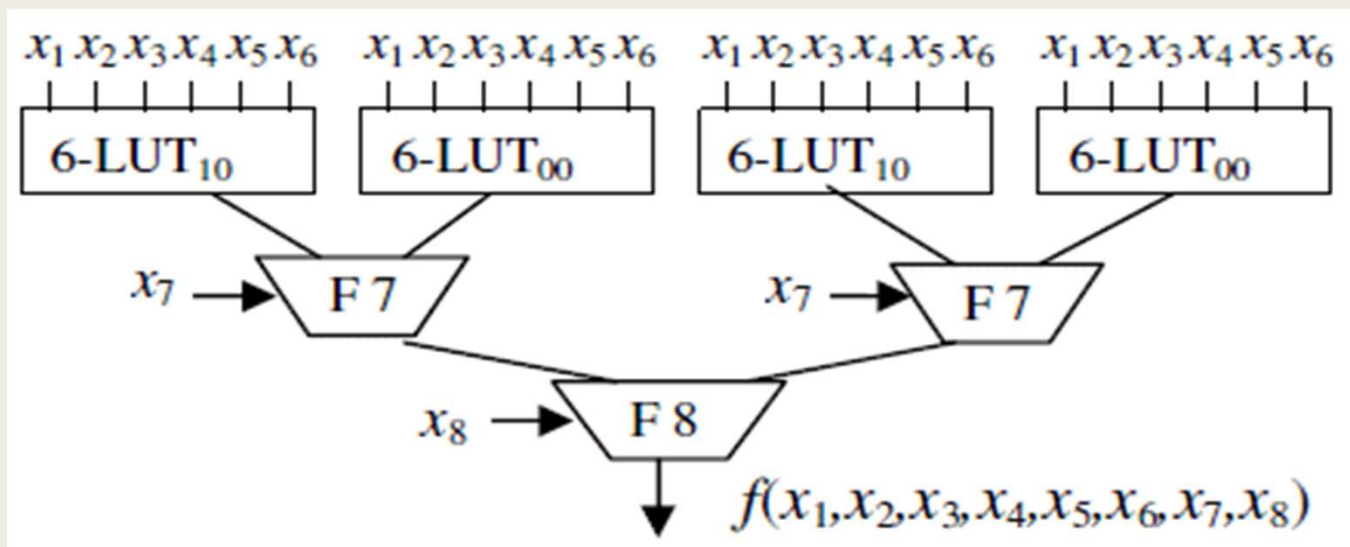
- A slice contains multiplexers that mux between LUT outputs (MUXFx)
- Virtex-4: MUXF5
- Virtex-5 and later: MUXF7, MUXF8



Logic optimization using MUXFx

- Example:
 - LUT4 architecture (Virtex4)
 - $O = I1 \& I2 \& I3 \& I4 \& I5 \Rightarrow 1 \text{ LUT}, 1 \text{ MUXF5}, 0.72\text{ns}$
- Use of MUXFx reduces LUT usage and routing requirements
- Local (in-Slice) routing -> more predictable performance

Logic optimization using MUXFx

 


Multiplexers vs First Index Decoders

- Example code:

```
always @*  
    if(A)  
        Out = E | F;  
    else if(B)  
        Out = E & F;  
    else if(C)  
        Out = E ^ F;  
    else if(D)  
        Out = ~E | F;  
    else Out = 1'bx;
```

Multiplexers vs First Index Decoders

 


Multiplexers vs. First Index Decoders

- The synthesis tool cannot always detect properties of the inputs of logic functions
 - Inputs are from pins
 - Inputs are from memories (Block or Distributed)
- Unconstrained version, for when we know {A,B,C,D} is one-hot:

```
assign sel1 = ~(A | B);  
assign sel0 = B | D;
```

```
always @*  
    case({sel1,sel0})  
        2'b00: Out = E | F;  
        2'b01: Out = E & F;  
        2'b10: Out = E ^ F;  
        2'b11: Out = ~E | F;  
    endcase
```


Multiplexers vs. First Index Decoders


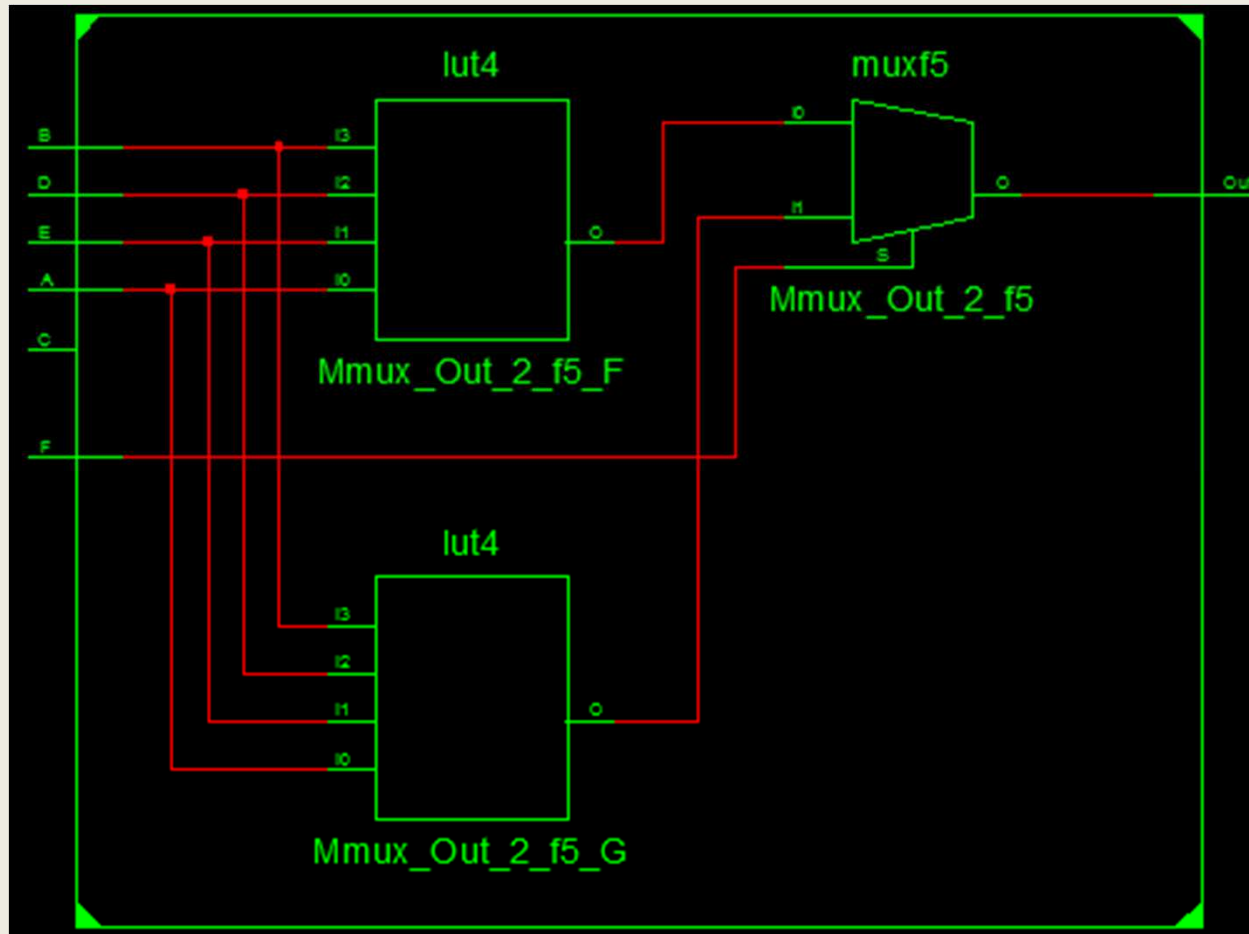


Exercise: Adder

- LUT6 Architecture (7-Series)
- Implement 4-bit adder optimally (carry-chain versus carry look-ahead)


Slice Arithmetic Resources

- Carry-chain adder implementation

  

Slice Arithmetic Resources

- Slice primitives: MUXCY, XORCY

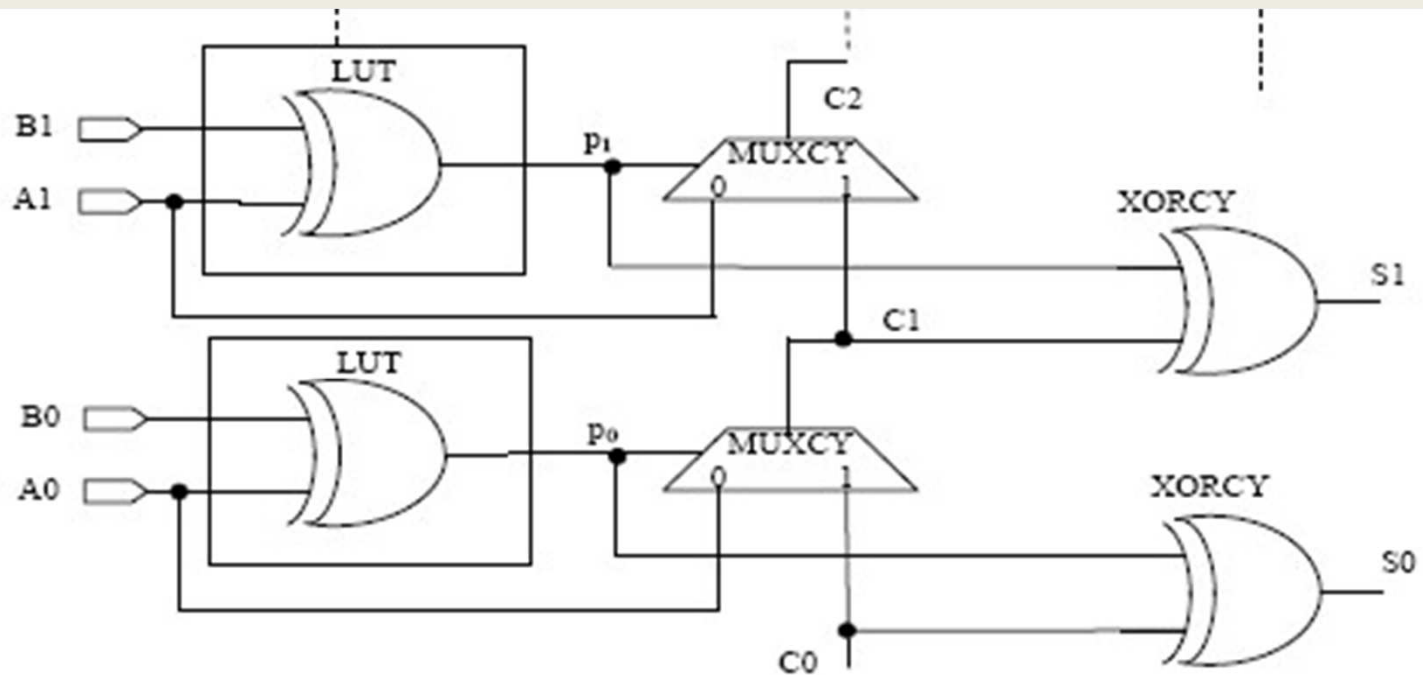

Selecting Adder Type

- [Analysis of various adder types](#)

(Design and Performance Analysis of Various Adders using Verilog; M. SaiKumar, P. Samundiswary)

- Ripple-carry (RCA) has hardware support in FPGA
- Carry-save (CSA) / Carry-look-ahead (CLA) are first choice for VLSI
- Assignment: compare RCA/CSA based Popcount
 - Implement Verilog for 16b input
 - Synthesize/Map
 - Record delay and LUT/Slice counts

Adder Inference

- Synthesis tools will infer RCA
- Multi-input adder implementation may be controlled through parentheses:
 - $E = (A+B)+(C+D)$ results in tree
 - $E = (A+(B+(C+D)))$ results in cascade

Optimization Example

- Implementing an “increment” instruction in a processor ALU in Virtex-4
- Behavioral description in ISE 14.2 yields bad results for the following code:

```
always @*  
    if(sel)        sum = a+b+carry_in;  
    else          sum = a+4'd1+carry_in;
```

- 12 Slices, 1.5ns delay. Can we do better?

Optimization Results

- Using LUT3s instead of LUT2s in the adder structure, we can hardcode a multiplexer that selects between operand b and constant “1” before XOR-ing with operand a
- The rest of the structure is identical (MUXCY, XORCY) and built with primitive instantiation
- Results: 2 Slices, 1ns delay

Slice Registers

- Latch/FlipFlop primitives available within the Slice
- Available control signals: Set/Reset, Clock Enable, Clock
- Asynchronous/Synchronous Set/Reset
 - Set/Reset typically refers to synchronous
 - Clear/Preset refers to asynchronous
- Primitives: $FD\{R/S/RS/C/P\}\{E\}$

Slice Registers

	Synchronous	Asynchronous
Set	<pre>always @(posedge clock) if(set) q<=1; else q<=d;</pre>	<pre>always @(posedge clock or posedge set) if(set) q<=1; else q<=d;</pre>
Reset	<pre>always @(posedge clock) if(reset) q<=0; else q<=d;</pre>	<pre>always @(posedge clock or negedge reset) if(set) q<=0; else q<=d;</pre>


Using Clock Enables

- Control signal priority determines implementation of the Flip-Flop primitive

Example 1: Set before CE	Example 2: CE before Set
<pre>always @(posedge clk) if(set) q<=1; else if(ce) q<=d;</pre>	<pre>always @(posedge clk) if(ce) if(set) q<=1; else q<=d;</pre>

Using Clock Enables

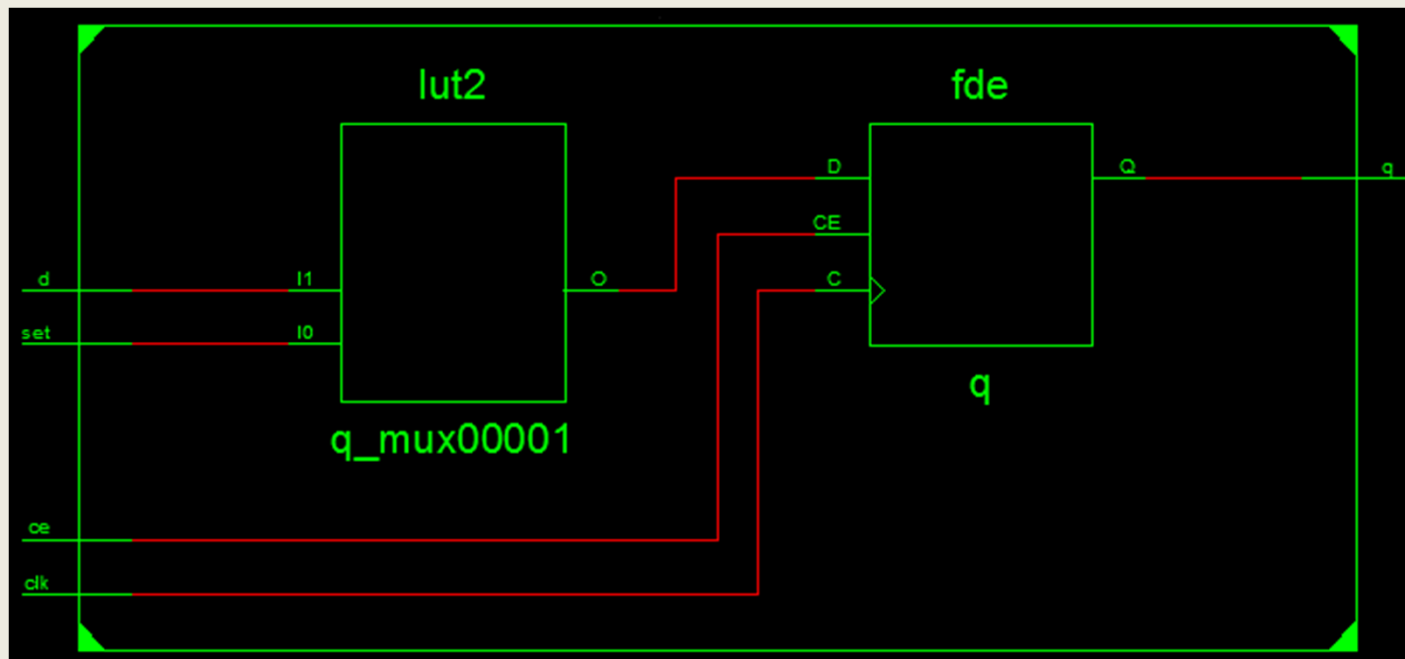- Example 1 Results: FDSE
- Example 2 Results: FDE + LUT




Using Clock Enables

- Flip-Flop primitives are architecture dependent
- Example:

```
always @(posedge clk)
    if(reset) q<=0;
    else if(set) q<=1;
    else if(ce) q <= d;
```

Using Clock Enables

- Spartan-3: FDRSE
- Virtex-6: LUT+FDR

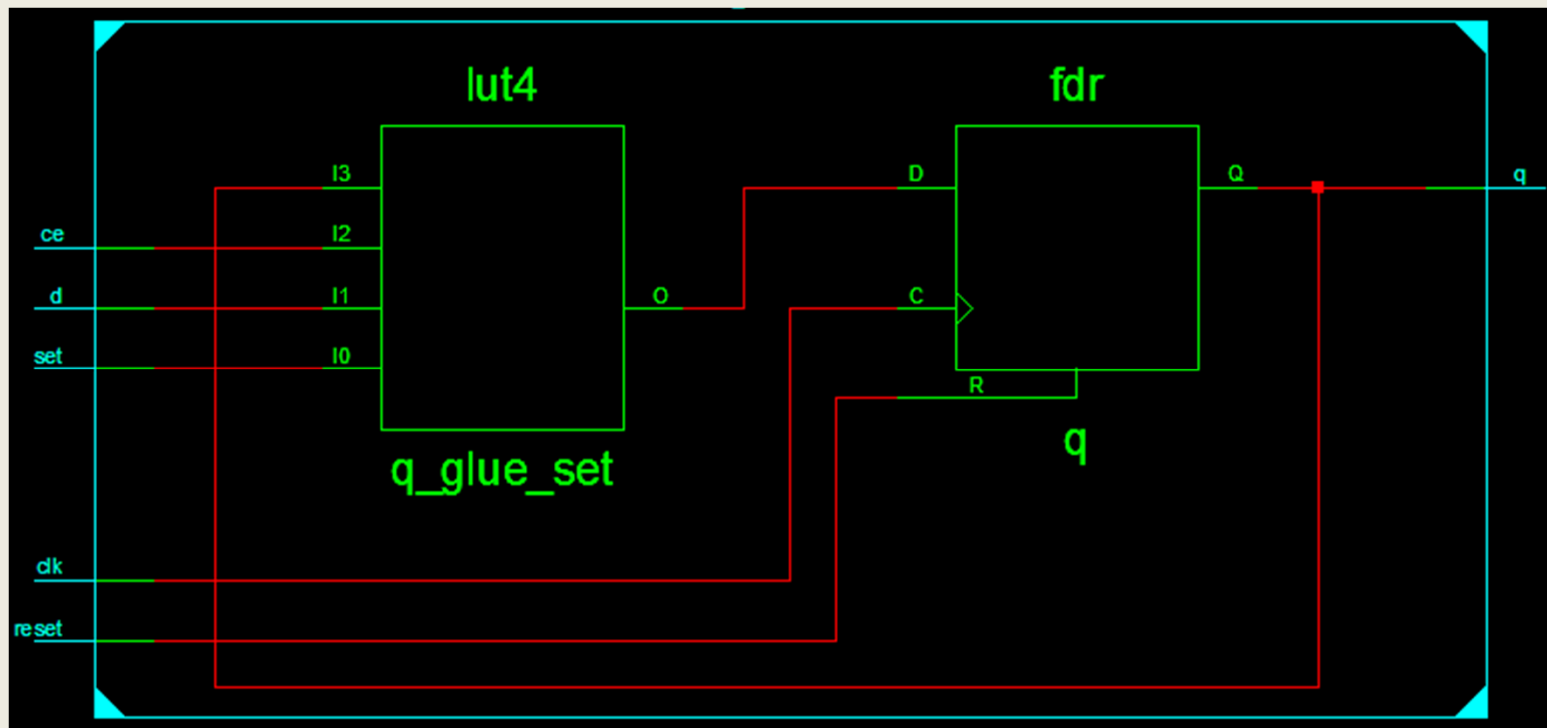


Using Clock Enables

- Another example:

```
always @(posedge clk)
    if(set) q<=1;
    else if(reset) q<=0;
    else if(ce) q <= d;
```

Using Clock Enables

 

Async vs Sync Resets

- Asynchronous resets
 - Act immediately
 - Are clock-independent
 - Induce timing hazards
- Synchronous resets
 - Ports can be used to minimize logic
 - Predictable

Global Resets

- We use global resets to:
 - Get the circuit into a known state at power-up
 - Initialize simulations properly (!)
- Global resets have to be routed to S/R pins of the Flip-Flop
- FPGAs include a dedicated global set-reset net for post-configuration initialization (GSR)

Using the GSR

```
STARTUP_VIRTEX6 #(
.PROG_USR("FALSE") // Activate program event security feature
)
STARTUP_VIRTEX6_inst (
.CFGCLK(CFGCLK), // 1-bit Configuration main clock output
.CFGMCLK(CFGMCLK), // 1-bit Configuration internal oscillator clock output
.DINSPI(DINSPI), // 1-bit DIN SPI PROM access output
.EOS(EOS), // 1-bit Active high output signal indicating the End Of Configuration.
.PREQ(PREQ), // 1-bit PROGRAM request to fabric output
.TCKSPI(TCKSPI), // 1-bit TCK configuration pin access output
.CLK(CLK), // 1-bit User start-up clock input
.GSR(GSR), // 1-bit Global Set/Reset input (GSR cannot be used for the port name)
.GTS(GTS), // 1-bit Global 3-state input (GTS cannot be used for the port name)
.KEYCLEARB(KEYCLEARB), // 1-bit Clear AES Decrypter Key input from Battery-Backed RAM (BBRAM)
.PACK(PACK), // 1-bit PROGRAM acknowledge input
.USRCCLKO(USRCCLKO), // 1-bit User CCLK input
.USRCCLKTS(USRCCLKTS), // 1-bit User CCLK 3-state enable input
.USRDONEO(USRDONEO), // 1-bit User DONE pin output control
.USRDONETS(USRDONETS) // 1-bit User DONE 3-state enable output
);
```

Avoid Latches!

- Latches are most commonly generated by unterminated control sequences
 - Missing “else” statements in “if” clauses
 - Missing “default” statements in “case” clauses
- To avoid over-constraining the logic, use “x” values in your “else” and “default” statements