

# FPGA Clocking

- Clock-related issues:
  - distribution
  - generation (frequency synthesis)
  - Deskew
  - multiplexing
  - run-time programming
  - domain crossing
- Clock-related constraints

# Clock Distribution


- Device split into halves (top/bottom) and clock regions (rectangular, uniform size)
- Different clock buffer types:
  - BUFG can clock any FF within the top or bottom of device (top/bottom BUFGs)
  - BUFR clocks a single clock region
  - BUFMR clocks up to 3 clock regions
  - BUFH clock a horizontal clock spine within a region

# FPGA Clocking


- Clock generation (frequency synthesis)
  - Uses “Clock Management Tiles” which consist of:
    - PLL/DCM (Frequency Synthesis)
    - MMCM (Advanced PLL with phase control)
  - Clock input from PCB must use “Clock capable pins” of FPGA
    - Differential pairs
    - Single-ended clocks always use P side
 
# Frequency Synthesis

- Common use case: generate all design clocks from single input clock (crystal oscillator)




# Frequency Synthesis with MMCM

 

 
# Frequency Synthesis with MMCM

MMCM Input Block: VCO frequency generator

- $F_{VCO} = F_{CLKIN} * (M/D)$
- $F_{VCO}$  is limited, not all M/D values are valid



# Frequency Synthesis with MMCM

 


Output divider block:

- Phase shift
- Frequency division

PLL lacks the following:

- Variable Phase Tap
- CLKOUTxB
- CLKFBOUTB
- Fractional dividers


# Frequency Synthesis with MMCM

 

```
MMCME2_BASE #(
    .CLKFBOUT_MULT_F(), // (2.000-64.000)
    .CLKOUTx_DIVIDE(), // (1-128)
    .CLKOUT0_DIVIDE_F(), // (1.000-128.000)
    .CLKOUTx_DUTY_CYCLE() // (0.01-0.99)
    .DIVCLK_DIVIDE(), // (1-106)
) MMCME2_BASE_inst (
    .CLKOUTx(),
    .CLKOUTxB(),
    .CLKFBOUT(),
    .CLKFBOUTB(),
    .LOCKED(),
    .CLKIN1(),
    .PWRDWN(),
    .RST(),
    .CLKFBIN());
```

 
# Clock deskew with MMCM

- Skew is delay in clock arrival at FFs, which is caused by clock routing (buffers, wires)


 
# Clock deskew with MMCM

- Use clock buffer in same clock region of FPGA to drive CLKFBIN
- Output clock buffers must be in the same clock region relative to their function:
  - BUFG same half
  - BUFH same clock region



# Dynamic MMCM Reconfiguration



- MMCMs have run-time (dynamic) reconfiguration ports
- Reconfigurable parameters:
  - Phase
  - Divide Counters
  - Duty cycle
- Configuration through multiple registers and addressable access port (see XAPP 888 in further reading)

# Clock Multiplexing

- Many applications require clock multiplexing:
  - In-circuit debugging (to avoid domain crossing)
  - Dynamic frequency scaling
  - Clock redundancy (switch away from dead clock)
- FPGA clock multiplexers (2:1) implemented with BUFGMUX\_CTRL primitive
  
# Clock Multiplexing

- Clock switch latency: max 3 clock cycles of the slower clock
- Glitchless output




# Clock-Related Constraints

- Timing constraints:
  - Period: guides timing analysis with regard to a periodic signal (clock)
    - NET "<clock\_name>" TNM\_NET = "<group\_name>;"
    - TIMESPEC <spec\_name> = PERIOD "<group\_name>"<period> <unit> HIGH/LOW <percentage> %;
  - OFFSET IN/OUT
  - FROM:TO

# Clock domain crossing

 - Problem: direct crossing leads to metastability




# Clock domain crossing

- FPGAs have rapid average metastability recovery (ps)
- But recovery is unbounded (probability is non-null that the metastable state will last a given time  $T$ )
- Design goal: achieve a desired MTBF, given the recovery parameters of the flip-flop

 
# Clock domain crossing

- Synchronizer: Multiple FFs at the receiving end guard against metastability
- Number of FFs a function of desired MTBF and ratio of clock frequencies


 
# Clock domain crossing

- Register output from source domain for more predictable timing (increased MTBF)




# Clock domain crossing

- 2FF synchronizers work well when destination clock is faster than source clock (signal will remain stable for at least one destination clock cycle)
- Fast-to-slow crossing requires closed-loop synchronizer with handshake
 
# Clock domain crossing

- Closed-loop: Control signal crosses into clock domain 2, then back into clock domain 1, and is checked against the reference (high latency)



# Further Reading

- [Article: Tim Behne, FPGA Clock Schemes](#)
- [Xilinx 7-Series Clock Resources User Guide](#)
- [XAPP888: MMCM and PLL Dynamic Reconfiguration](#)
- [Cliff Cummings: Clock Domain Crossing](#)
- [XAPP94: Metastability Recovery](#)
- [Xilinx: FPGA Design Techniques](#)
- [SOC Central: Clock Domain Crossing Demystified](#)